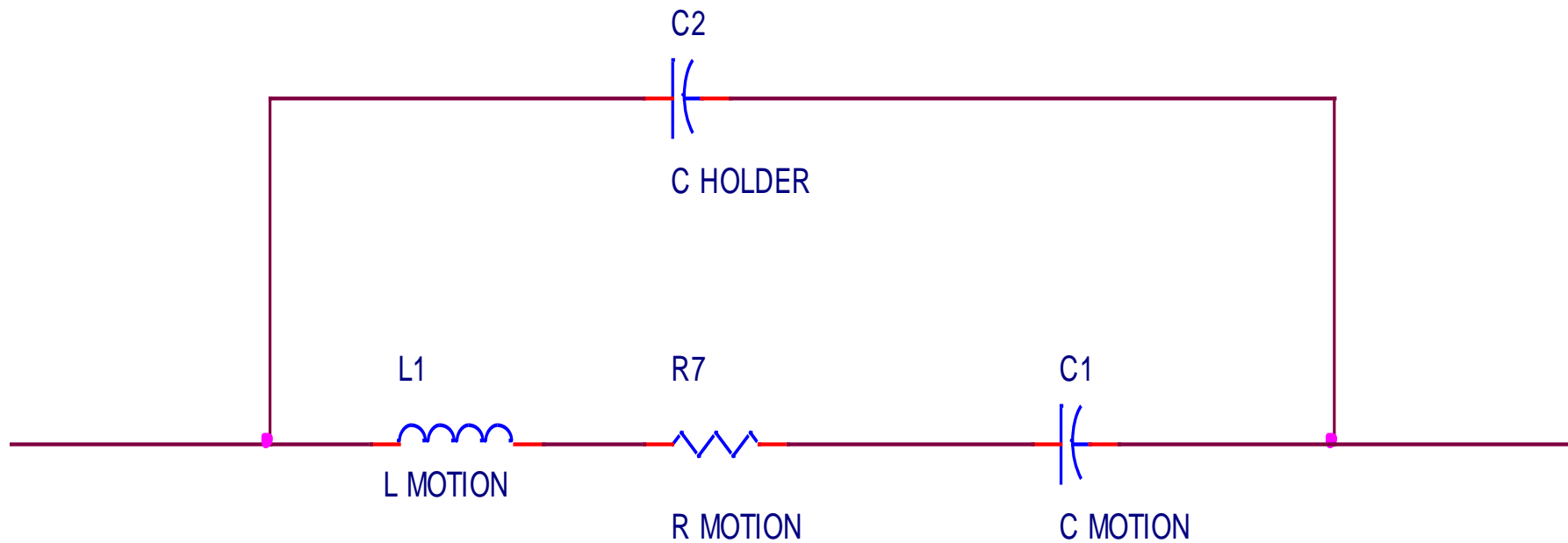


How to Measure a Quartz Crystal

Brian Straup N5YC

For the Roadrunners Microwave Group Austin Summerfest 8/8/15


What does a Crystal Look Like




What do we REALLY need to Measure

- ▶ Four Basic Parameters
- ▶ Series Resistance
- ▶ Holder Capacitance (Plates or Deposited Metal on crystal)
- ▶ Motion Inductance Determines the Frequency
- ▶ Motion Capacitance Determines the frequency


Why do we need to measure all that ?

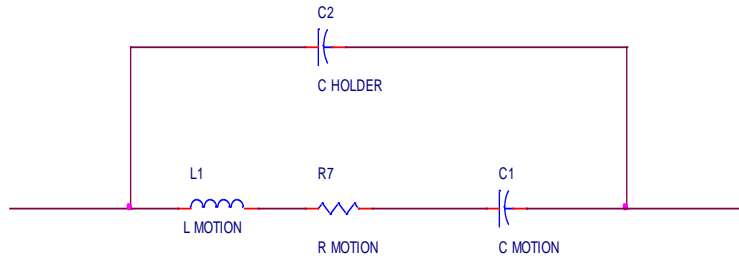

=

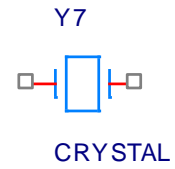


CRYSTAL

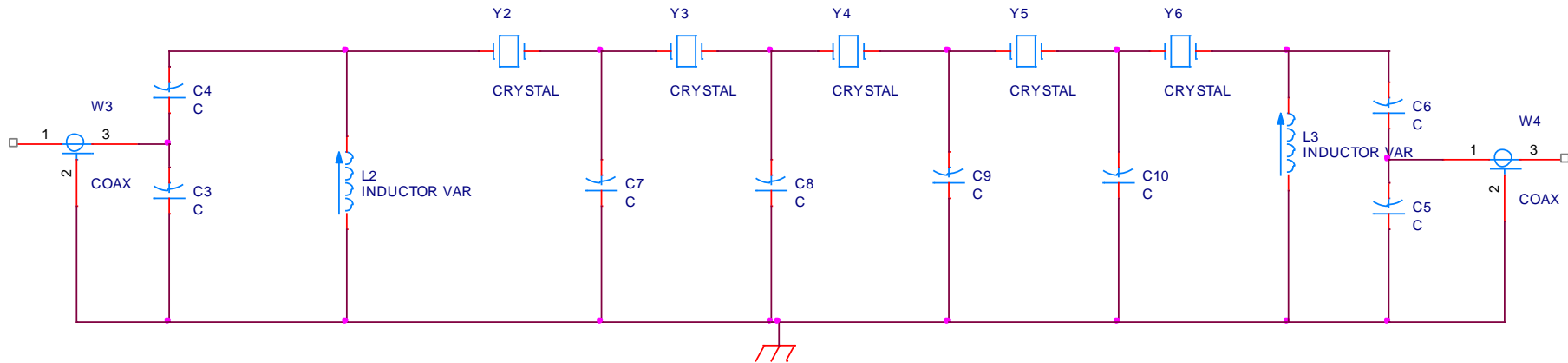


12.228 MHz SHELF FILTER

TEST SETUP

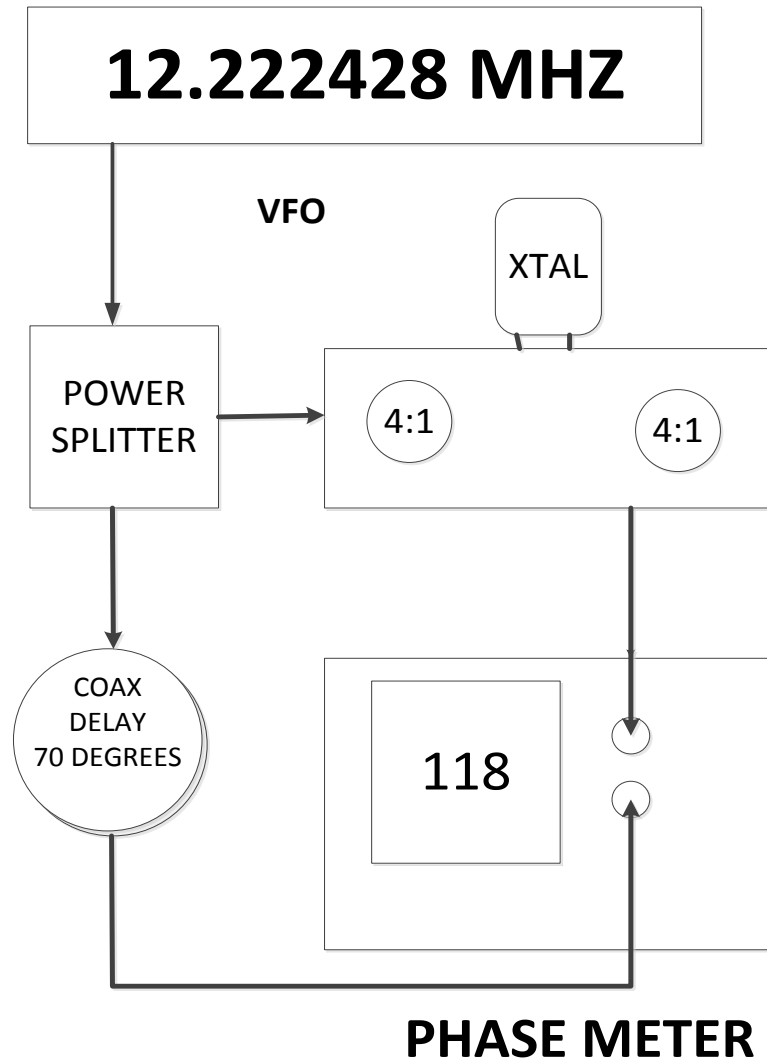

DUT SCHEMATIC

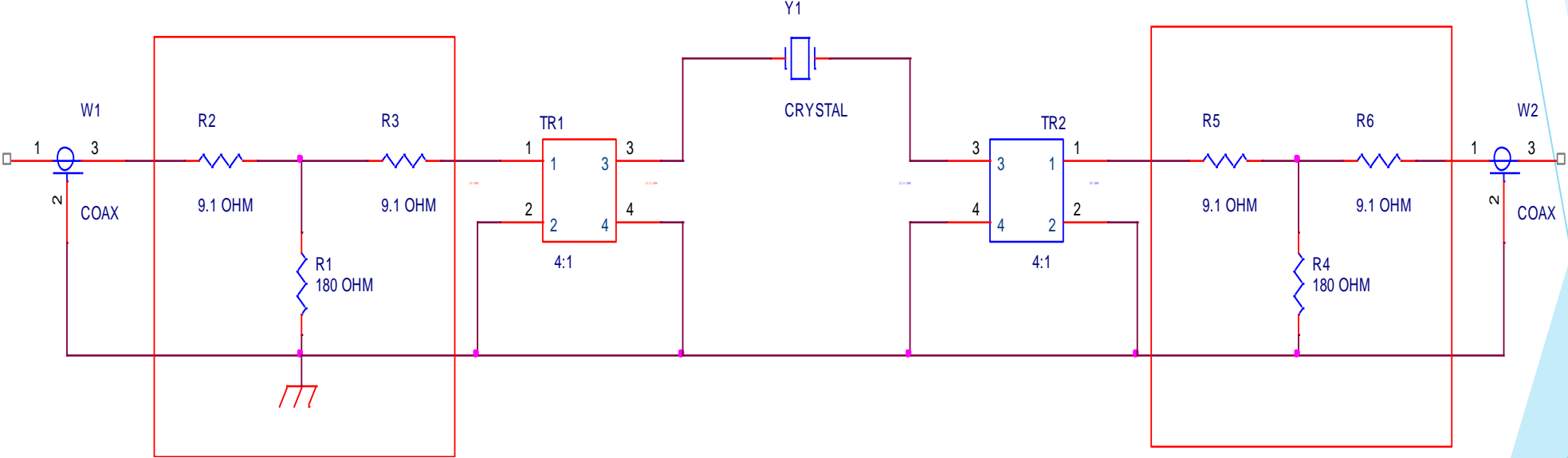

DUT Description

- ▶ 12.5 OHM Impedance
- ▶ 3 DB Pads to provide Impedance match
- ▶ Broad Band 4:1 ferrite Balun. Two windings #28 WW wire 14T
- ▶ 3DB pad T Configuration 9.1 Ohm and 180 Ohm

Power Splitter

- ▶ 6 DB Attenuation per port
- ▶ Less sensitive to load variations
- ▶ Trifilar windings forming a center tapped secondary
- ▶ Provides two paths 180 Degrees out of phase

Inside the DUT Box



VFO

- ▶ Signal Generator Needs 1 HZ resolution
- ▶ 0 to +10 DBM Output
- ▶ Using a VFO with Si570 chip



Phase Meter

- ▶ Based on W1GHZ Ratiometer Project
- ▶ Works on Phase Differences between 20 and 160 Degrees
- ▶ 20' of RG-58 provides about 70 degrees of phase shift
- ▶ Puts the phase differences in the active region of the meter
- ▶ Arduino Processor and TFT display

System Calibration

- ▶ Place a short in place of the crystal
- ▶ Set the VFO to the crystal's manufactured frequency. The actual crystal frequency may be +/- several KHz either way.
- ▶ Note the phase angle on the phase meter, this will be 0 degrees reference
- ▶ Replace the phase meter with a milliwatt power meter or calibrated 50 ohm volt meter. Take a reading. This will be 0DB attenuation for measuring the series resistance.
- ▶ Install Crystal and reconnect the Phase meter.

Finding the Crystal's Resonate Frequency

- ▶ Adjust the VFO frequency until the Phase reading matches the reading with the short. This will be 0 Degrees or resonance of the crystal. In my case with the roll of coax I had in the shop, the phase difference was 73.85 degrees.



Measure Crystal Attenuation

- ▶ Reconnect the power meter and take a reading with the crystal at resonance. The maximum voltage (power) may be at a different point, but only the resonate voltage counts.
- ▶ Save this attenuation for later. My case the attenuation was 1.1DB
- ▶ Save the VFO frequency for later 12.222420 MHz was my reading


Measurement at - 45 Degree

- ▶ Reconnect the Phase Meter
- ▶ Adjust the VFO until the Phase is 45 Degrees lower than the reference phase.
In my case 28 Degrees (73 - 45) Write down this Frequency



Go The Other Way

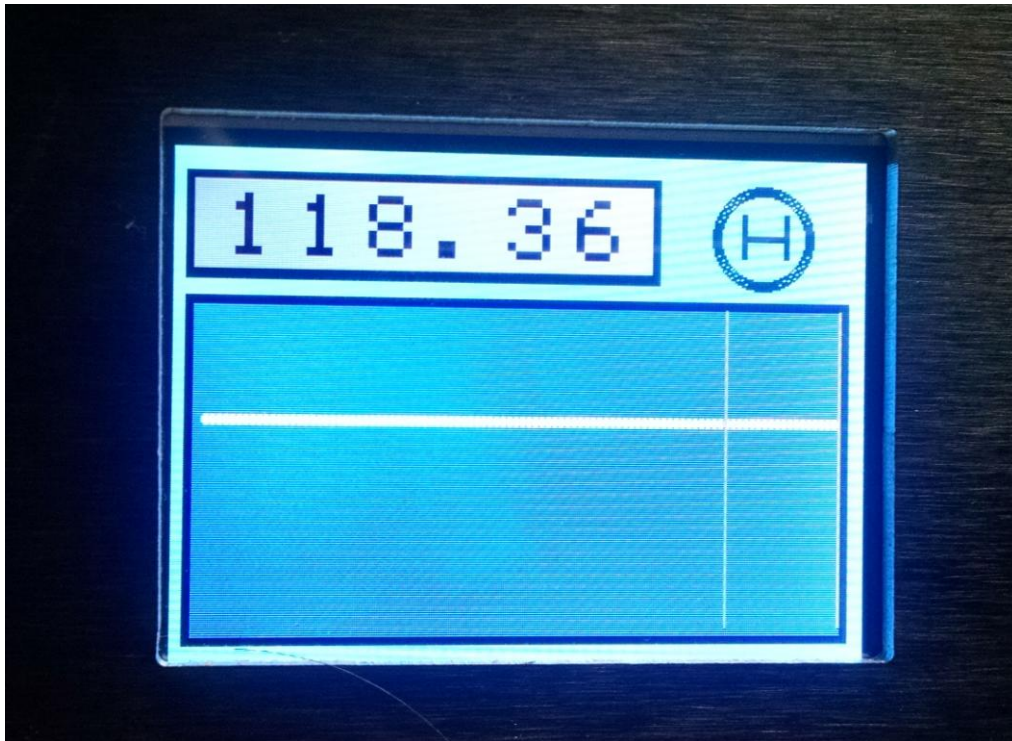- ▶ Adjust Phase for + 45 Degrees $73+45 = 118$
- ▶ Save this frequency



Numbers you need to know

- ▶ $\tan (45) = 1$
- ▶ System Impedance = 12.5 Ohm
- ▶ Attenuation 1.1 DB
- ▶ F_s = Center Frequency 12.222420 MHz
- ▶ $F-45$ = 12.222928 MHz
- ▶ $F+45$ = 12.222156 MHz
- ▶ Delta Frequency = 772 Hz

Motion Resistance

The relationship between attenuation and series resistance is:

$$R_M = 2R_L \left(10^{\frac{\alpha}{20}} - 1 \right)$$

Where

R_M is the motional resistance

R_L is the source and load resistance seen by the crystal (a function of the test fixture)

α is the loss in dB

$$RM = 2 \times 12.5 * [10^{(1.1/20)} - 1]$$

$$RM = 3.539083 \text{ Ohm}$$

$$REFF = 2RL + RM$$

$$REFF = 2 \times 12.5 + 3.54 \quad \text{or } 28.54 \text{ Ohms}$$

Motion Values

$$C_M = \frac{\Delta f(\pm\theta)}{2\pi f_R^2 R_{EFF} \tan(\theta)}$$

$$CM = (772) / [2 * 3.1415 * 12222420 * 12222420 * 1]$$

$$CM = 2.92696E-14 \text{ Farads or } .29 \text{ Femto Farads}$$


$$L_M = \frac{R_{EFF}}{2\pi\Delta f(\pm\varphi)} \tan(\theta)$$

$$LM = 28.54 / [2 * 3.14159 * 772]$$

$$LM = 0.005793075 \text{ or } 5.79 \text{ mH}$$

Last but Not Least

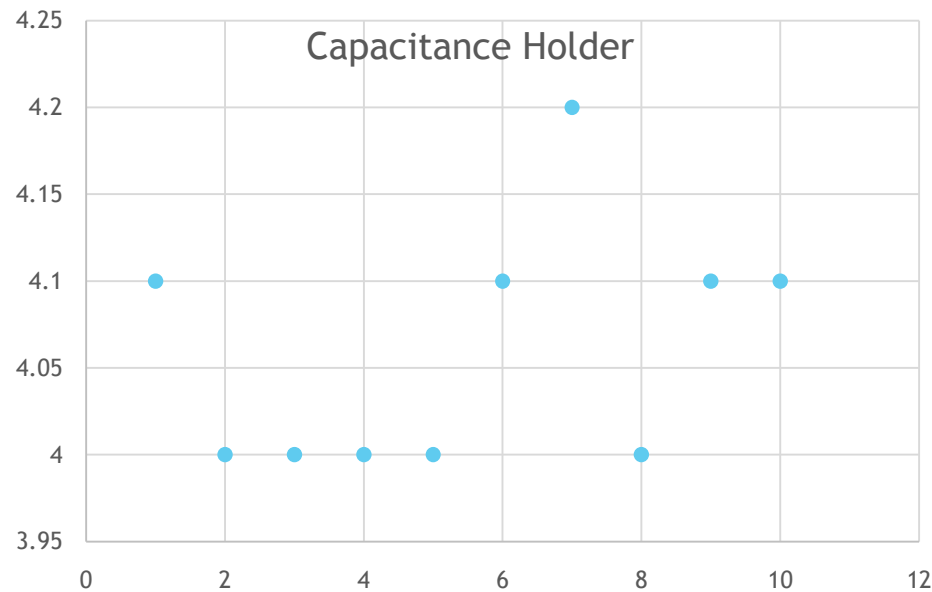- ▶ Cp or Parallel Capacitance
- ▶ Measure in a LRC bridge. I made a holder for 4 crystals to measure in parallel
- ▶ Be sure to take in account of any fixture capacitance
- ▶ In my case Most of the crystals measured close to 4 pF




All Measurements In Place

- ▶ All four major parameters are now measured
- ▶ Sanity Check $1 / (2 * 3.14259 * \text{SQRT}(LM * CM)$ Resonate Frequency
- ▶ $1 / (2 * 3.4159 * \text{SQRT}(0.005793075 * 2.92696\text{E-}14)$
- ▶ $F_{\text{calculated}} = 12222420 \text{ Hz}$
- ▶ $F_{\text{measured}} = 12222420 \text{ Hz}$

OK Now What

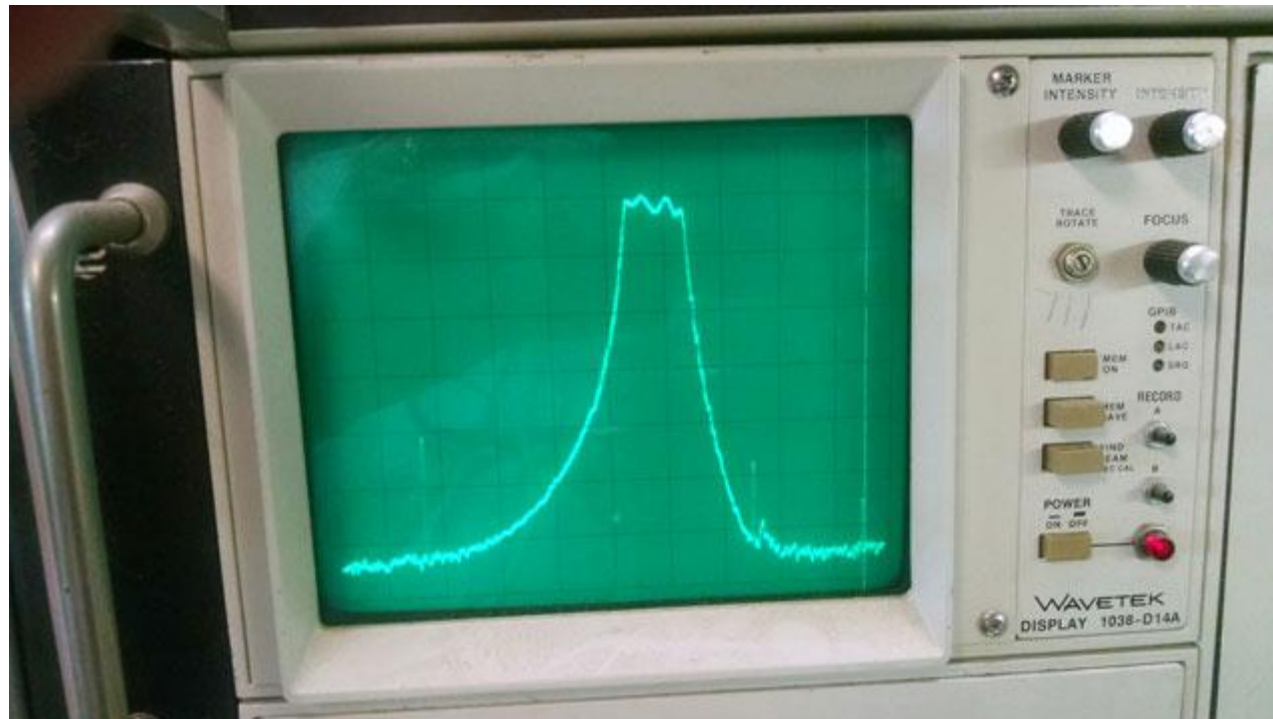- ▶ Tune in next presentation on Lattice filters
- ▶ First sample built 5 KHz bandwidth with ~ 1DB ripple after tuning



Really Good Reference

- ▶ <http://www.cliftonlaboratories.com/Documents/Crystal%20Motional%20Parameters.pdf>
- ▶ Phase Meter W1GHZ.org Antenna ratiometer